

**For:sanjay**

**Printed on:Wed, Sep 30, 1998 10:56:06**

**Document:lab5**

**Last saved on:Wed, Sep 30, 1998 10:54:57**

# Lab 5: Body Effect

## Introduction

The purpose of this lab is to investigate the body effect and the variation in the threshold voltages of NMOS devices with body effect.

## Part A

Set up a string of three series connected NMOS devices M1, M2, M3. The source of M1 is at ground and the drain of M3 is connected to a variable voltage source VDD. Use aspect ratios of  $2.4\mu/0.6\mu$  for all the transistors. The drain and the gate of all the transistors are shorted together. Short the bulk terminals to the respective source terminals. Vary the voltage VDD from 0 to 5v.

Obtain plots for the gate voltages of M1, M2 and M3 and the drain current (current flowing from VDD to ground). As VDD is varied from 0 to 5v, current starts to flow once the threshold for all the 3 transistors are reached. At the onset of current flow, identify on the plot  $V_{s1}$ ,  $V_{s2}$ ,  $V_{s3}$  (the source voltages of the corresponding transistors), and the values of  $V_{t1}$ ,  $V_{t2}$ ,  $V_{t3}$ .

## Part B

Repeat Part A tying the bulk terminal of all devices to ground (instead of tying them to their corresponding source terminals). Obtain plots and identify the voltages as outlined in Part A.

## To Turn In

1. Plots for parts A and B with the source and threshold voltages for transistors marked
2. Your spice stimulus files and circuit files for each.
3. Answer to the following question:

There is a reference voltage of VDD. Show an implementation to obtain  $V_{DD}/2$  from the reference voltage source using a series string of pmos transistors. Turn in a schematic of your circuit with all the terminal connections clearly marked.