



Contents

Preface ix

To Students About To Study Digital Design ix

To Instructors of Digital Design ix

How to Use This Book xii

 RTL-Focused Approach xii

 Traditional Approach with Some Reordering xii

 Traditional Approach xiii

Acknowledgements xiii

About the Cover xiv

About the Author xiv

Reviewers and Evaluators xv

▶ CHAPTER 1

Introduction 1

1.1 Digital Systems in the World Around Us 1

1.2 The World of Digital Systems 4

 Digital versus Analog 4

 Digital Encodings and Binary Numbers—0s and
 1s 9

1.3 Implementing Digital Systems:

 Microprocessors versus Digital Circuits 22

 Software on Microprocessors: The Digital
 Workhorse 22

 Digital Design—When Microprocessors Aren't
 Good Enough 26

1.4 About this Book 28

1.5 Exercises 29

▶ CHAPTER 2

Combinational Logic Design 35

2.1 Introduction 35

2.2 Switches 36

 Electronics 101 36

 The Amazing Shrinking Switch 37

2.3 The CMOS Transistor 40

2.4 Boolean Logic Gates—Building Blocks for
 Digital Circuits 43

 Boolean Algebra and its Relation to Digital
 Circuits 43

 AND, OR, & NOT Gates 46

 Building Simple Circuits Using Gates 49

2.5 Boolean Algebra 52

 Notation and Terminology 53

 Some Properties of Boolean Algebra 55

 Complementing a Function 60

2.6 Representations of Boolean Functions 61

 Equations 62

 Circuits 62

 Truth Tables 62

 Converting among Boolean Function

 Representations 64

 Standard Representation and Canonical Form 68

 Multiple-Output Combinational Circuits 71

2.7 Combinational Logic Design Process 73

2.8 More Gates 80

 NAND & NOR 80

 XOR & XNOR 81

 Interesting Uses of these Additional Gates 82

 Completeness of NAND and of NOR 82

 Number of Possible Logic Gates 83

2.9 Decoders and Muxes 84

 Decoders 84

 Multiplexers (Muxes) 86

2.10 Additional Considerations 91

 Nonideal Gate Behavior—Delay 91

 Active Low Inputs 92

 Demultiplexers and Encoders 93

 Schematic Capture and Simulation 93

2.11 Combinational Logic Optimizations
 and Tradeoffs (See Section 6.2) 95

2.12 Combinational Logic Description Using
 Hardware Description Languages (See
 Section 9.2) 95

2.13 Chapter Summary 96

2.14 Exercises 96

▶ **CHAPTER 3****Sequential Logic Design: Controllers 105**

- 3.1** Introduction 105
- 3.2** Storing One Bit—Flip-Flops 106
 - Feedback—The Basic Storage Method 106
 - Basic SR Latch 107
 - Level-Sensitive SR Latch 111
 - Level-Sensitive D Latch—A Basic Bit Store 112
 - Edge-Triggered D Flip-Flop—A Robust Bit Store 113
 - Clocks and Synchronous Circuits 117
 - Basic Register—Storing Multiple Bits 120
- 3.3** Finite-State Machines (FSMs) 122
 - Mathematical Formalism for Sequential Behavior—FSMs 124
 - How to Capture Desired System Behavior as an FSM 129
- 3.4** Controller Design 132
 - Standard Controller Architecture for Implementing an FSM as a Sequential Circuit 132
 - Controller (Sequential Logic) Design Process 133
 - Converting a Circuit to an FSM (Reverse Engineering) 140
 - Common Mistakes when Capturing FSMs 142
 - FSM and Controller Conventions 145
- 3.5** More on Flip-Flops and Controllers 146
 - Non-Ideal Flip-Flop Behavior 146
 - Flip-Flop Reset and Set Inputs 149
 - Initial State of a Controller 150
 - Non-Ideal Controller Behavior: Output Glitches 151
- 3.6** Sequential Logic Optimizations and Tradeoffs (See Section 6.3) 153
- 3.7** Sequential Logic Description Using Hardware Description Languages (See Section 9.3) 153
- 3.8** Product Profile—Pacemaker 153
- 3.9** Chapter Summary 156
- 3.10** Exercises 157

▶ **CHAPTER 4****Datapath Components 167**

- 4.1** Introduction 167
- 4.2** Registers 168
 - Parallel-Load Register 168
 - Shift Register 173
 - Multifunction Registers 175
 - Register Design Process 179
- 4.3** Adders 181
 - Adder—Carry-Ripple Style 183
- 4.4** Comparators 191
 - Equality (Identity) Comparator 191
 - Magnitude Comparator—Carry-Ripple Style 192
- 4.5** Multiplier—Array-Style 195
- 4.6** Subtractors and Signed Numbers 196
 - Subtractor for Positive Numbers Only 196
 - Representing Negative Numbers: Two's Complement Representation 200
 - Building a Subtractor Using an Adder and Two's Complement 203
 - Detecting Overflow 205
- 4.7** Arithmetic-Logic Units—ALUs 207
- 4.8** Shifters 210
 - Simple Shifters 211
 - Barrel Shifter 214
- 4.9** Counters and Timers 215
 - Up-Counter 216
 - Up/Down-Counter 217
 - Counter with Load 218
 - Timers 222
- 4.10** Register Files 225
- 4.11** Datapath Component Tradeoffs (See Section 6.4) 230
- 4.12** Datapath Component Description Using Hardware Description Languages (See Section 9.4) 230
- 4.13** Product Profile: An Ultrasound Machine 230
 - Functional Overview 231
 - Digital Circuits in an Ultrasound Machine's Beamformer 234
 - Future Challenges in Ultrasound 237
- 4.14** Chapter Summary 237
- 4.15** Exercises 238

▶ **CHAPTER 5****Register-Transfer Level (RTL) Design 247**

- 5.1** Introduction 247
- 5.2** High-Level State Machines 248
- 5.3** RTL Design Process 255
 - Step 2A—Creating a Datapath using Components from a Library 259
 - Step 2B—Connecting the Datapath to a Controller 262
 - Step 2C—Deriving the Controller’s FSM 263
- 5.4** More RTL Design 264
 - Additional Datapath Components for the Library 264
 - RTL Design Involving Register Files or Memories 265
 - RTL Design Pitfall Involving Storage Updates 271
 - RTL Design Involving a Timer 272
 - A Data-Dominated RTL Design Example 275
- 5.5** Determining Clock Frequency 278
- 5.6** Behavioral-Level Design: C to Gates (Optional) 281
- 5.7** Memory Components 285
 - Random Access Memory (RAM) 286
 - Bit Storage in a RAM 288
 - Using a RAM 290
 - Read-Only Memory (ROM) 292
 - ROM Types 294
 - Using a ROM 297
 - The Blurring of the Distinction between RAM and ROM 299
- 5.8** Queues (FIFOs) 299
- 5.9** Multiple Processors 303
- 5.10** Hierarchy—A Key Design Concept 305
 - Managing Complexity 305
 - Abstraction 306
 - Composing a Larger Component from Smaller Versions of the Same Component 307
- 5.11** RTL Design Optimizations and Tradeoffs (See Section 6.5) 309
- 5.12** RTL Design Using Hardware Description Languages (See Section 9.5) 310

- 5.13** Product Profile: Cell Phone 310
 - Cells and Basestations 310
 - How Cellular Phone Calls Work 311
 - Inside a Cell Phone 312

5.14 Chapter Summary 316**5.15** Exercises 317▶ **CHAPTER 6****Optimizations and Tradeoffs 325**

- 6.1** Introduction 325
- 6.2** Combinational Logic Optimizations and Tradeoffs 327
 - Two-Level Size Optimization Using Algebraic Methods 327
 - A Visual Method for Two-Level Size Optimization—K-Maps 329
 - Don’t Care Input Combinations 336
 - Automating Two-Level Logic Size Optimization 339
 - Multilevel Logic Optimization—Performance and Size Tradeoffs 348
- 6.3** Sequential Logic Optimizations and Tradeoffs 351
 - State Reduction 351
 - State Encoding 354
 - Moore versus Mealy FSMs 360
- 6.4** Datapath Component Tradeoffs 365
 - Faster Adders 365
 - Smaller Multiplier—Sequential (Shift-and-Add) Style 375
- 6.5** RTL Design Optimizations and Tradeoffs 377
 - Pipelining 377
 - Concurrency 380
 - Component Allocation 381
 - Operator Binding 382
 - Operator Scheduling 383
 - Moore versus Mealy High-Level State Machines 386
- 6.6** More on Optimizations and Tradeoffs 386
 - Serial versus Concurrent Computation 386
 - Optimizations and Tradeoffs at Higher versus Lower Levels of Design 387
 - Algorithm Selection 388
 - Power Optimization 389

- 6.7 Product Profile: Digital Video Player/Recorder 393
 - Digital Video Overview 393
 - DVD—One Form of Digital Video Storage 393
 - MPEG-2 Video Encoding—Sending Frame Differences Using I-, P-, and B-Frames 395
 - Transforming to the Frequency Domain for Further Compression 396
- 6.8 Chapter Summary 402
- 6.9 Exercises 403

▶ CHAPTER 7

Physical Implementation on ICs 413

- 7.1 Introduction 413
- 7.2 Manufactured IC Types 414
 - Full-Custom Integrated Circuits 414
 - Semicustom (Application-Specific) Integrated Circuits—ASICs 415
- 7.3 Off-the-Shelf Programmable IC Type—FPGA 423
 - Lookup Tables 424
 - Mapping a Circuit among Multiple Lookup Tables 426
 - Programmable Interconnects (Switch Matrices) 432
 - Configurable Logic Block 434
 - Overall FPGA Architecture 436
- 7.4 Other Off-the-Shelf IC Types 438
 - Off-the-Shelf Logic (SSI) IC 438
 - Simple Programmable Logic Device (SPLD) 441
 - Complex Programmable Logic Device (CPLD) 445
 - FPGA-to-Structured-ASIC Flows 445
- 7.5 IC Tradeoffs, Trends, and Comparisons 446
 - Tradeoffs Among IC Types 447
 - IC Technology Trend—Moore’s Law 448
 - Relative Popularity of IC Types 450
 - ASSPs 450
 - IC Types versus Processor Varieties 451
 - FPGAs alongside Microprocessors 452
- 7.6 Product Profile: Giant LED-Based Video Display with FPGAs 453
- 7.7 Chapter Summary 457
- 7.8 Exercises 457

▶ CHAPTER 8

Programmable Processors 461

- 8.1 Introduction 461
- 8.2 Basic Architecture 462
 - Basic Datapath 462
 - Basic Control Unit 465
- 8.3 A Three-Instruction Programmable Processor 469
 - A First Instruction Set with Three Instructions 469
 - Control Unit and Datapath for the Three-Instruction Processor 471
- 8.4 A Six-Instruction Programmable Processor 475
 - Extending the Instruction Set 475
 - Extending the Control Unit and Datapath 476
- 8.5 Example Assembly and Machine Programs 478
- 8.6 Further Extensions to the Programmable Processor 480
 - Instruction Set Extensions 480
 - Input/Output Extensions 481
 - Performance Extensions 481
- 8.7 Chapter Summary 482
- 8.8 Exercises 483

▶ CHAPTER 9

Hardware Description Languages 487

- 9.1 Introduction 487
- 9.2 Combinational Logic Description Using Hardware Description Languages 489
 - Structure 489
 - Combinational Behavior 494
 - Testbenches 498
- 9.3 Sequential Logic Description Using Hardware Description Languages 501
 - Register 501
 - Oscillator 503
 - Controllers 505
- 9.4 Datapath Component Description Using Hardware Description Languages 509
 - Full-Adders 509

- Carry-Ripple Adders 511
- Up-Counter 514
- 9.5** RTL Design Using Hardware Description Languages 517
 - High-Level State Machine of the Laser-Based Distance Measurer 517
 - Controller and Datapath of the Laser-Based Distance Measurer 523
- 9.6** Chapter Summary 532
- 9.7** Exercises 532

▶ APPENDIX A

Boolean Algebras 537

- A.1** Boolean Algebra 537
- A.2** Switching Algebra 538
- A.3** Important Theorems in Boolean Algebra 540
- A.4** Other Examples of Boolean Algebras 545
- A.5** Further Readings 545

▶ APPENDIX B

Additional Topics in Binary Number Systems 547

- B.1** Introduction 547
- B.2** Real Number Representation 547
- B.3** Fixed Point Arithmetic 550
- B.4** Floating Point Representation 551
 - The IEEE 754-1985 Standard 552
- B.5** Exercises 556

▶ APPENDIX C

Extended RTL Design Example 557

- C.1** Introduction 557
- C.2** Designing the Soda Dispenser Controller 558
- C.3** Understanding the Behavior of the Soda Dispenser Controller and Datapath 562

