

3

Coding Styles for Logic Building Blocks

This chapter shows different coding styles for logic building blocks such as decoders and priority encoders. A typical coding style and a recommended coding style are presented for each building block.

The examples in this chapter are parameterizable: They can be modified for any bit-width. Therefore, they may appear more complex than examples written for a specific bit-width.

Decoder

Example 3-1 and Example 3-2 show Verilog and VHDL with a frequently used coding style for decoders. The input is used as an index to the output in these examples.

Example 3-1 Verilog for Decoder Using Indexing

```
module decoder_index (in1, out1);
  parameter N = 8;
  parameter log2N = 3;
  input [log2N-1:0] in1;
  output [N-1:0] out1;
  reg [N-1:0] out1;
  always @(in1)
  begin
    out1 = 0;
    out1[in1] = 1'b1;
  end
endmodule
```

Example 3-2 VHDL for Decoder Using Indexing

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity decoder38_index is
  generic (N: natural := 8; log2N: natural := 3);
  port (in1: in std_logic_vector(log2N-1 downto 0);
        out1: out std_logic_vector(N-1 downto 0));
end decoder38_index;

architecture one of decoder38_index is
  signal in1_int: natural range 0 to N-1;
begin
  in1_int <= CONV_INTEGER(in1);
  process(in1_int)
  begin
    out1 <= (others => '0');
    out1(in1_int) <= '1';
  end process;
end one;
```

Example 3-3 and Example 3-4 show an alternative coding style for decoders, using a `for` loop.

Example 3-3 Verilog for Decoder Using Loop

```

module decoder38_loop (in1, out1);
parameter N = 8;
parameter log2N = 3;
input [log2N-1:0] in1;
output [N-1:0] out1;
reg [N-1:0] out1;
integer i;

always @(in1)
begin
    for(i=0;i<N;i=i+1)
        out1[i] = (in1 == i);
end
endmodule

```

Example 3-4 VHDL for Decoder Using Loop

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity decoder_loop is
generic (N: natural := 8; log2N: natural := 3);
port (in1: in std_logic_vector(log2N-1 downto 0);
      out1: out std_logic_vector(N-1 downto 0));
end decoder_loop;

architecture one of decoder_loop is
signal in1_int: natural range 0 to N-1;
begin
    in1_int <= CONV_INTEGER(in1);
    process(in1_int)
    begin
        out1 <= (others => '0');
        for i in 0 to N-1 loop
            if (in1_int = i) then
                out1(i) <= '1';
            end if;
        end loop;
    end process;
end one;

```

Table 3-1 and Figure 3-1 show timing results for different-size decoders, using the decoder coding styles described in the preceding examples.

Table 3-1 Timing Results for Decoder Coding Styles

Input Address Width	3	4	5	6	7	8
Index	0.64	0.86	1.33	1.52	2.11	2.37
Loop	0.64	0.86	1.33	1.57	1.98	2.10

Figure 3-1 Decoder Timing Results Versus Address Width

 


Table 3-2 and Figure 3-2 show area results for the decoder coding styles described in the preceding examples.

Table 3-2 Area Results for Decoder Coding Styles

Input Address Width	3	4	5	6	7	8
Index	18	29	61	115	195	583
Loop	18	30	61	116	195	346

Figure 3-2 Decoder Area Versus Address Width


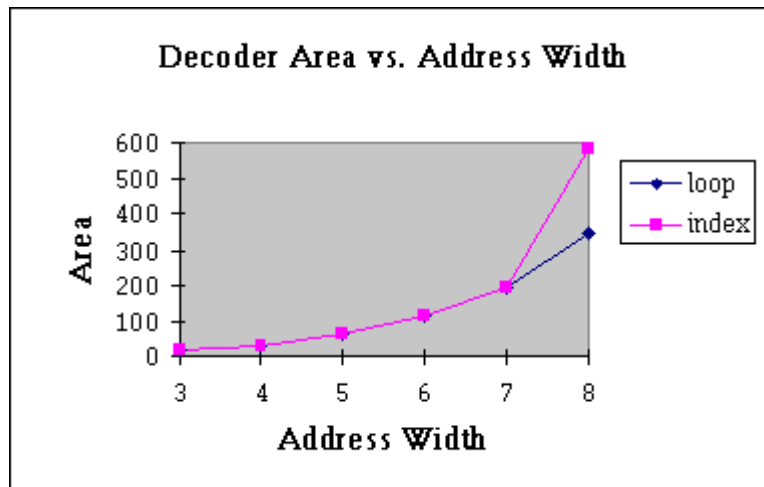


Table 3-3 and Figure 3-3 show compile time for the decoder coding styles described previously.

Table 3-3 Compile Time (Seconds) for Decoder Coding Styles

Input Address Width	3	4	5	6	7	8
Index	2	3	11	18	58	132
Loop	16	13	42	163	946	9000

Figure 3-3 Decoder Compile Times Versus Address Width

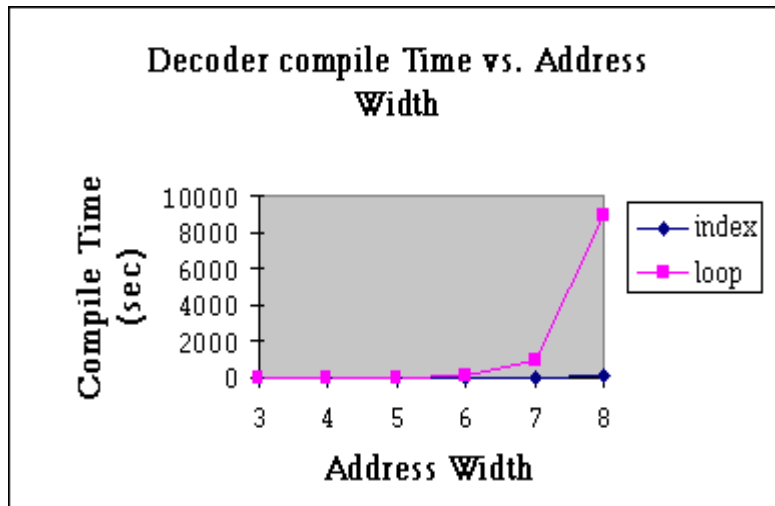

In conclusion, Example 3-1 and Example 3-2, using indexing, are more concise and readable than the other examples and have faster compile time overall. On the other hand, Example 3-3 and Example 3-4, using a `for` loop, give slightly better timing results for address widths larger than 6 and better area results for address widths larger than 7. Select a specific coding style based on design requirements (decoder size required and so on).

Priority Encoder

Example 3-5 and Example 3-6 show Verilog and VHDL versions of an 8-to-3 priority encoder using a `for` loop. A function is used in the Verilog example to calculate the highest priority index. A procedure is used in the VHDL example because procedures can have multiple return values.

Example 3-5 Verilog for Priority Encoder Using Loop Starting With Lowest Priority Bit

```

module priority_low_high (A, P, F);
parameter N = 8;
parameter log2N = 3;
input [N-1:0] A; //Input Vector
output [log2N-1:0] P; // High Priority Index
output F; // Found a one?
reg [log2N-1:0] P;
reg F;

function [log2N:0] priority;
input [N-1:0] A;
reg F;
integer I;
begin
    F = 1'b0;
    priority = {3'b0, F};
    for (I=0; I<N; I=I+1)
        if (A[I])
            begin
                F = 1'b1;
                priority = {I, F}; // Override previous index
            end
end
endfunction

always @(A)
begin
    {P, F} <= priority(A);
end
endmodule

```

Example 3-6 is the equivalent VHDL example. This example uses a function, `log2`, to calculate log base 2 and a procedure to find the highest priority index.

Example 3-6 VHDL for Priority Encoder Using Loop Starting With Lowest Priority Bit

```

package pri_pack is
    function log2(A: natural) return natural;
end pri_pack;

package body pri_pack is
    function log2(A: natural) return natural is
    begin
        for I in 1 to 30 loop -- Works for up to 32 bit integers
            if (2**I > A) then
                return(I-1);
            end if;
        end loop;
        return(30);
    end;
end pri_pack;

library IEEE;
use work.pri_pack.all;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity priority_low_high is
    generic(N: natural := 3);
    port (A: in std_logic_vector(2**N - 1 downto 0);
          P: out std_logic_vector(N-1 downto 0);
          F: out std_logic);
end priority_low_high;

architecture a of priority_low_high is
    procedure priority(A: in std_logic_vector;      -- Input Vector
                      P: out std_logic_vector;    -- High Priority Index
                      F: out std_logic) isb       -- Found a one?
    constant WIDTH: NATURAL := A'length;
    constant LOG_WIDTH: NATURAL := log2(WIDTH);
    begin
        P := CONV_STD_LOGIC_VECTOR(CONV_UNSIGNED(0, LOG_WIDTH),
                                   LOG_WIDTH); -- Set output default
        F := '0';
        for I in 0 to WIDTH-1 loop
            if(A(I) = '1') then-- If found a '1'
                P := CONV_STD_LOGIC_VECTOR(CONV_UNSIGNED(I, LOG_WIDTH),
                                             LOG_WIDTH); -- Override previous index
                F := '1';
            end if;
        end loop;
    end;
end architecture a;

```



```

end priority;


begin
  process(A)
    variable PV: std_logic_vector(N-1 downto 0);
    variable FV: std_logic;

    begin
      priority(A, PV, FV);
      P <= PV;
      F <= FV;
    end process;
end a;

```

Example 3-4 shows the chain structure implied by the HDL in Example 3-5 and Example 3-6.

Figure 3-4 Chain Structure for Priority Encoder

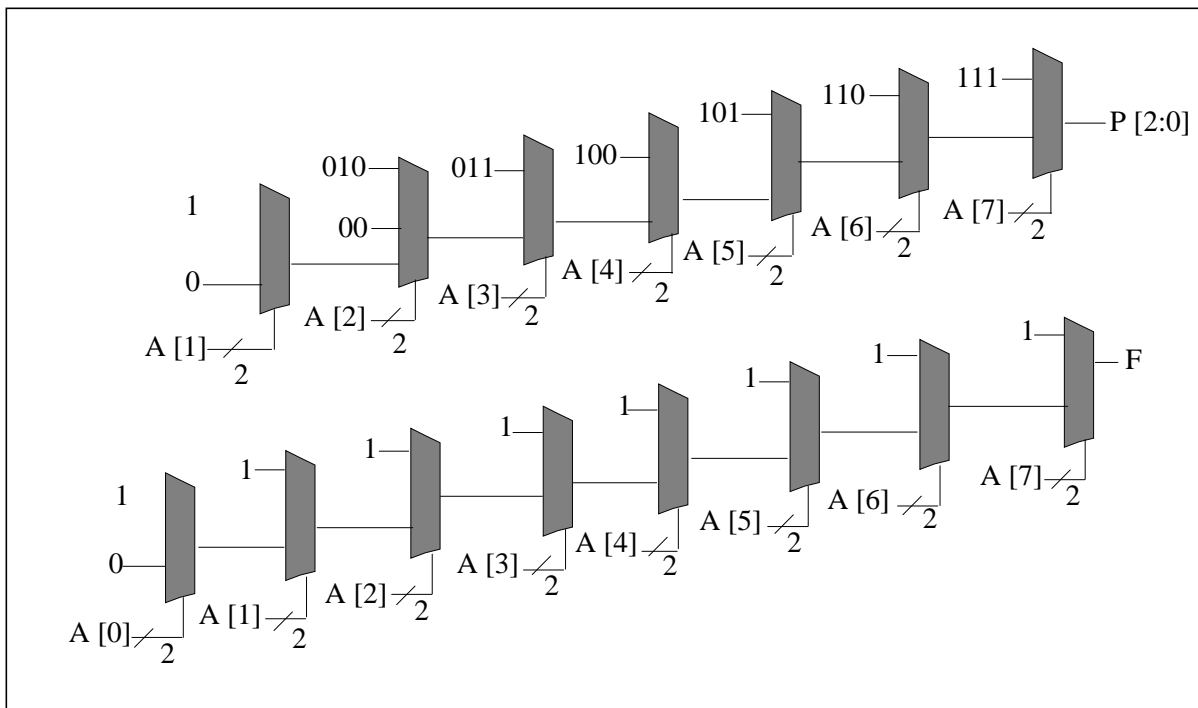

Example 3-5 and Example 3-6 can be modified to create a tree structure. Tree structures generally result in better performance. Only the VHDL tree structure is shown in Example 3-7.

Using recursion in VHDL gives you the ability to create a priority encoder in a tree structure. Example 3-7 uses recursive procedure calls to generate a tree structure for a priority encoder.

Example 3-7 VHDL for Priority Encoder Tree

```

package pri_pack2 is
    function log2(A: integer) return integer;
    function max(A,B: integer) return integer;
end pri_pack2;

package body pri_pack2 is
    function max(A,B: integer) return integer is
    begin
        if(A<B) then
            return(B);
        else
            return(A);
        end if;
    end;

    function log2(A: integer) return integer is
    begin
        for I in 1 to 30 loop-- Works for up to 32 bit integers
            if(2**I > A) then
                return(I-1);
            end if;
        end loop;
        return(30);
    end;
end pri_pack2;

library IEEE;
use IEEE.std_logic_1164.all;
use work.pri_pack2.all;

entity priority_tree is
    port (A: in std_logic_vector(2**N - 1 downto 0);
          P: out std_logic_vector(N-1 downto 0);
          F: out std_logic);
end priority_tree;

architecture a of priority_tree is

    procedure priority(A: in std_logic_vector;      -- Input Vector
                      P: out std_logic_vector;    -- High Priority Index
                      F: out std_logic) is        -- Found a one?
        constant WIDTH: INTEGER := A'length;
        constant LOG_WIDTH: INTEGER := log2(WIDTH);
        variable AT: std_logic_vector(WIDTH-1 downto 0);
        variable F1, F0: std_logic;
        variable PRET: std_logic_vector(LOG_WIDTH-1 downto 0);
        variable P1, P0, PT:std_logic_vector(max(LOG_WIDTH-2,0) downto 0);
    end procedure;
end architecture a;

```

```
begin
    AT := A;    -- Normalize array indices

    -- Handle Degenerate case of single input

    if(WIDTH = 1) then
        F := AT(0);

        -- This is the bottom of the recursion: a 2-bit priority encoder

    elsif(WIDTH = 2) then
        PRET(0) := AT(0);
        F := AT(1) or AT(0);

        if(F1 = '1') then    --If the first half had a '1', use its index
            PT := P1;
        else
            PT := P0;    -- Otherwise, use the second half's index
        end if;
        PRET := F1 & PT;    -- The result MSB is '1' if the first half
                            -- had a '1'.

    end if;
    P := PRET;
end priority;

begin
    process(A)
        variable PV: std_logic_vector(N-1 downto 0);
        variable FV: std_logic;
    begin
        priority(A, PV, FV);
        P <= PV;
        F <= FV;
    end process;
end a;
```

Table 3-4 shows timing results for different-size priority encoders using the coding styles described in the preceding example.

Table 3-4 Timing Results for Various Encoder Coding Styles

Output Width	2	3	4	5	6
low_high	0.51	1.29	1.85	3.93	6.00
tree	0.51	1.48	1.71	2.85	4.05

Table 3-5 shows area results for different-size priority encoders using the coding styles described previously.

Table 3-5 Area Results for Various Encoder Coding Styles

Output Width	2	3	4	5	6
low_high	17	43	101	227	536
tree	17	33	90	168	419

Figure 3-5 shows the tree structure implied by the HDL in Example 3-7 on page 3-11.

Figure 3-5 Tree Structure for Priority Encoder


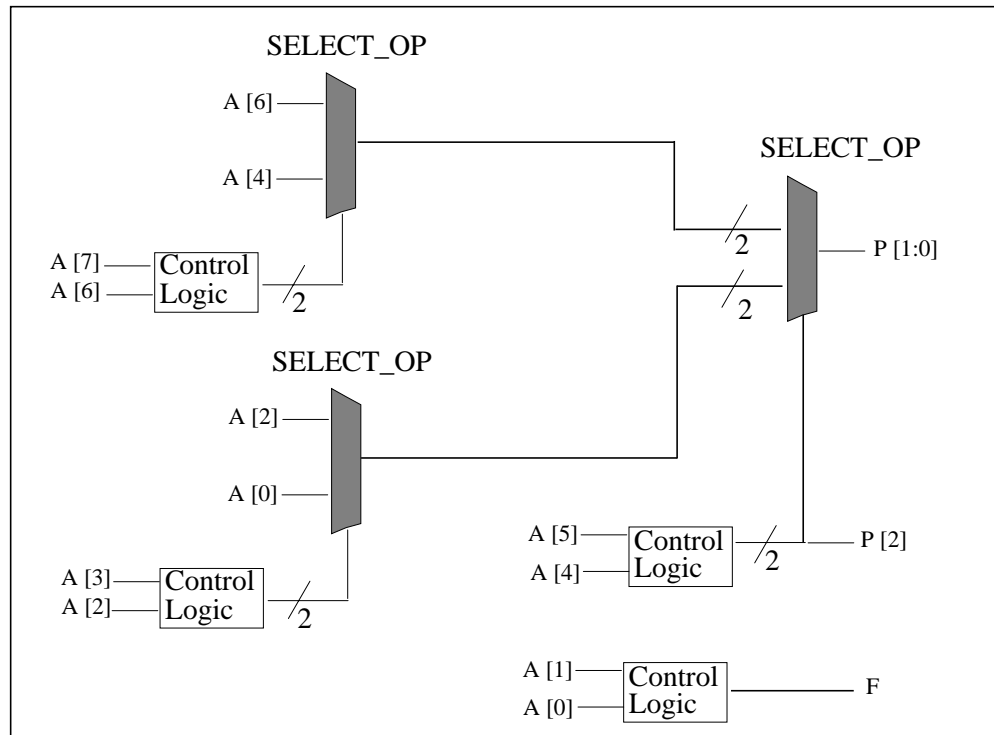


Table 3-6 and Figure 3-6 on page 3-15 show compile time in seconds for the various priority encoder coding styles.

Table 3-6 Compile Time (Seconds) for Various Encoder Coding Styles

Output Width	2	3	4	5	6
low_high	4	5	10	20	63
tree	3	4	7	13	27

Figure 3-6 Priority Encoder Compile Time Versus Output Width

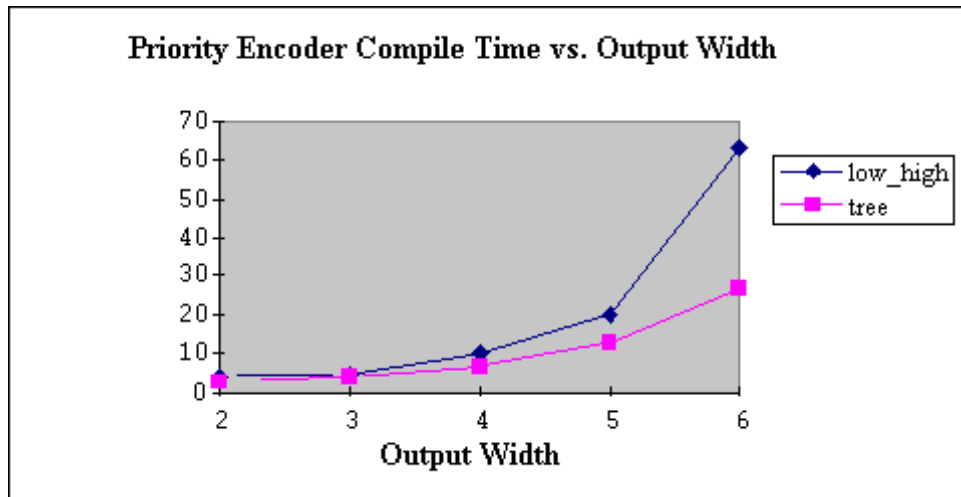

In conclusion, Example 3-5 on page 3-7 and Example 3-6 on page 3-8 using loops to override the previous index, are more concise and readable. But the tree version in Example 3-7 on page 3-11 is better with respect to timing, area, and compile time. In addition, the QOR difference between the two versions increases as the size of the priority encoder gets larger. For designs that are pushing performance, the tree version is the recommended coding style.

Reduction XOR

Reduction functions, especially reduction `XORs`, are frequently used in designs. Example 3-8 and Example 3-9 show Verilog and VHDL for a reduction `XOR` implemented in a chain structure. Chain structures are common for reduction functions.

Example 3-8 Verilog for Reduction XOR Chain

```
module XOR_reduce (data_in, data_out);
parameter N = 5;
input [N-1:0] data_in;
output data_out;
reg data_out;

function XOR_reduce_func;
input [N-1:0] data;
integer I;
begin
    XOR_reduce_func = 0;
    for (I = N-1; I >= 0; I=I-1)
        XOR_reduce_func = XOR_reduce_func ^ data[I];
end
endfunction

always @(data_in)
begin
    data_out <= XOR_reduce_func(data_in);
end
endmodule
```


Example 3-9 VHDL for Reduction XOR Chain

```

library IEEE;
use IEEE.std_logic_1164.all;

entity XOR_reduce is
generic (N: natural := 5);
port (data_in: in std_logic_vector(N-1 downto 0);
      data_out: out std_logic);
end XOR_reduce;


architecture one of XOR_reduce is
function XOR_reduce_func(data:std_logic_vector)return std_logic is
variable result : std_logic;
begin
    result := '0';
    for I in data'RANGE loop
        result := result XOR data(I);
    end loop;
    return result;
end;

begin
    data_out <= XOR_reduce_func(data_in);
end one;

```

Figure 3-7 shows the chain structure implied by the HDL in Example 3-8 and Example 3-9.

Figure 3-7 Chain Structure for Reduction XOR

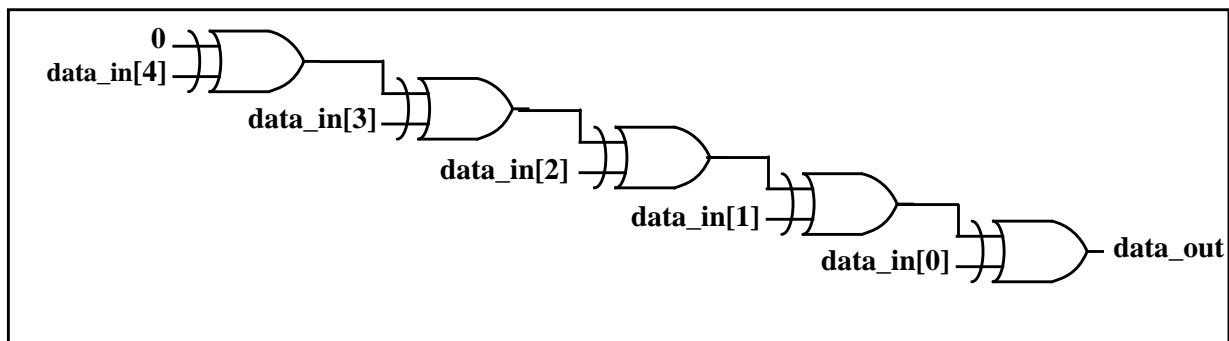

Example 3-10 on page 3-18 and Example 3-11 on page 3-20 show Verilog and VHDL, respectively, for the reduction XOR implemented in a tree structure.

Example 3-10 Verilog for XOR Tree

```
module XOR_tree(data_in, data_out);
parameter N = 5;
parameter logN = 3;
input[N-1:0] data_in;
output data_out;
reg data_out;

function even;
input [31:0] num;
begin
    even = ~num[0];
end
endfunction

function XOR_tree_func;
input [N-1:0] data;
integer I, J, K, NUM;
reg [N-1:0] temp, result;
begin
    temp[N-1:0] = data_in[N-1:0];
    NUM = N;
    for (K=logN-1; K>=0; K=K-1)
    begin
        J = (NUM+1)/2;
        J = J-1;
        if (even(NUM))
            for (I=NUM-1; I>=0; I=I-2)
            begin
                result[J] = temp[I] ^ temp[I-1];
                J = J-1;
            end
        else
            begin
                for (I=NUM-1; I>=1; I=I-2)
                begin
                    result[J] = temp[I] ^ temp[I-1];
                    J = J-1;
                end
            end
        result[0] = temp[0];
    end
endfunction
```

```
        end
        temp[N-1:0] = result[N-1:0];
        NUM = (NUM+1)/2;
    end
    XOR_tree_func = result[0];
end
endfunction

always @(data_in)
begin
    data_out <= XOR_tree_func(data_in);
end
endmodule
```

The VHDL version shown in Example 3-11 uses recursion to build a tree.

Example 3-11 VHDL for XOR Tree


```
library IEEE;
use IEEE.std_logic_1164.all;

entity XOR_tree is
generic (N: natural := 4);
port (data_in: in std_logic_vector(N downto 0);
      data_out: out std_logic);
end XOR_tree;

architecture one of XOR_tree is
function XOR_tree_func(data: std_logic_vector) return std_logic is
variable UPPER_TREE, LOWER_TREE: std_logic;
variable MID, LEN: natural;
variable result: std_logic;
variable i_data: std_logic_vector(data'LENGTH-1 downto 0);
begin
    i_data := data;
    LEN := i_data'LENGTH;
    if LEN = 1 then
        result := i_data(i_data'LEFT);
    elsif LEN = 2 then
        result := i_data(i_data'LEFT) XOR i_data(i_data'RIGHT);
    else
        MID := (LEN + 1)/2 + i_data'RIGHT;
        UPPER_TREE := XOR_tree_func(i_data(i_data'LEFT downto MID));
        LOWER_TREE := XOR_tree_func(i_data(MID-1 downto i_data'RIGHT));
        result := UPPER_TREE XOR LOWER_TREE;
    end if;
    return result;
end;
begin
    data_out <= XOR_tree_func(data_in);
end one;
```

Figure 3-8 shows the tree structure implied by the HDL in Example 3-10 and Example 3-11.

Figure 3-8 Tree Structure for Reduction XOR

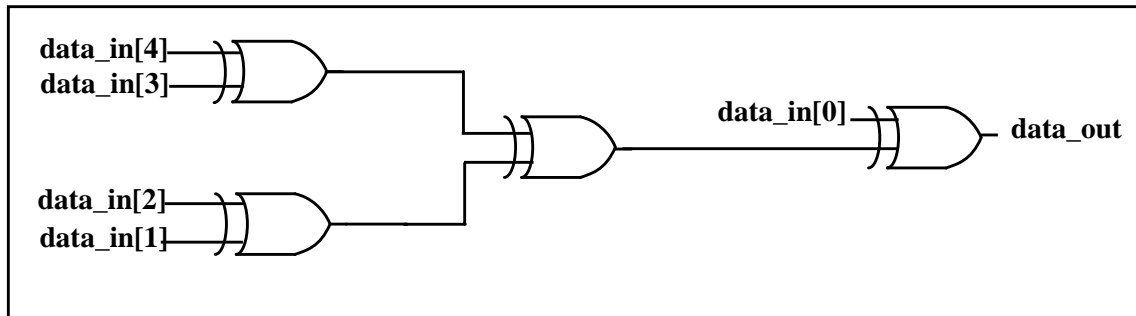

In conclusion, Design Compiler can convert the XOR chain structure to a tree structure during compile. However, it does not do so if the chain is used in a design that accesses intermediate points in the chain (outputs of gates along the chain). Therefore, it is best to start with the tree structure. OR chains with intermediate points, on the other hand, are converted to trees.

Multiplexer

Example 3-12 on page 3-22 and Example 3-13 on page 3-23 show, respectively, Verilog and VHDL for multiplexer chains. The structure implied by the HDL is a chain of multiplexing logic. This does not mean Design Compiler necessarily infers multiplexer cells for this logic. For information on how to get Design Compiler to map to multiplexer cells (especially large multiplexer cells) in the technology library, see the *HDL Compiler for Verilog Reference Manual*.

Example 3-12 Verilog for Multiplexer Chain

```
module mux_chain (sel, data_in, data_out);
parameter N = 5;
input [N-1:0] sel;
input [N:0] data_in;
output data_out;
reg data_out;

function mux_chain_func;
input [N-1:0] sel;
input [N:0] data_in;
reg [N-1:0] i_sel;
reg [N:0] i_data;
reg result;
integer I;
begin
    i_sel = sel;
    i_data = data_in;
    mux_chain_func = i_data[N];
    for (I = N-1; I >= 0; I=I-1)
        if (i_sel[I])
            mux_chain_func = i_data[I];
end
endfunction

always @(sel or data_in)
begin
    data_out <= mux_chain_func(sel, data_in);
end
endmodule
```

Example 3-13 VHDL for Multiplexer Chain

```
library IEEE;
use IEEE.std_logic_1164.all;


entity mux_chain is
generic (N: natural := 5);
port (sel: in std_logic_vector(N-1 downto 0);
      data_in: in std_logic_vector(N downto 0);
      data_out: out std_logic);
end mux_chain;

architecture one of mux_chain is
function mux_chain_func(sel, data: std_logic_vector)
return std_logic is
variable i_sel: std_logic_vector(sel'LENGTH-1 downto 0);
variable i_data: std_logic_vector(data'LENGTH-1 downto 0);
variable result: std_logic;
begin
    i_sel:= sel;
    i_data:= data;
    result:= i_data(i_data'LEFT);
    for I in i_sel'LENGTH - 1 downto 0 loop
        if i_sel(I) = '1' then
            result := i_data(I);
        end if;
    end loop;
    return result;
end;

begin
    data_out <= mux_chain_func(sel, data_in);
end one;
```

Figure 3-9 shows the structure implied by the HDL in Example 3-12 and Example 3-13.

Figure 3-9 Structure Implied by Multiplexer Chain Example

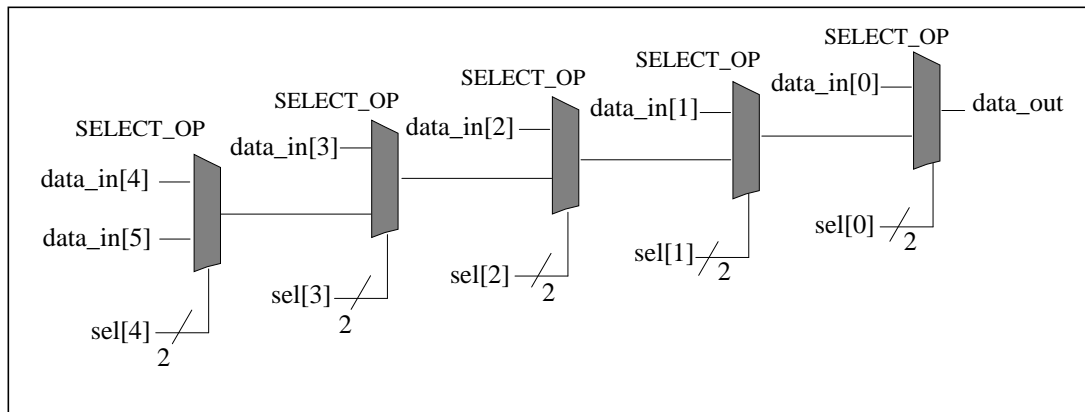

Example 3-14 and Example 3-15 show Verilog and VHDL that imply the same multiplexing functionality shown in Example 3-12 and Example 3-13 but in a tree structure rather than a chain structure.

Example 3-14 Verilog for Multiplexer Tree

```

module mux_tree(sel, data_in, data_out);
parameter N = 8;
parameter log2N = 3;
input [N-2:0] sel;
input [N-1:0] data_in;
output data_out;
reg data_out;

function even;
input [31:0] num;
begin
    even = ~num[0];
end
endfunction

function mux_2_1;
input sel;
input [1:0]data;

begin
    if (sel)
        mux_2_1 = data[0];
    else
        mux_2_1 = data[1];
end
endfunction

function mux_tree_func;
input [N-2:0] sel;
input [N-1:0] data_in;
reg [N-1:0] i_sel, temp_sel;
reg [N-1:0] i_data, result;
integer I, J, K, S;
integer TREE_DEPTH;
integer SEL_LEN, DATA_LEN;

begin
    i_data[N-1:0] = data_in[N-1:0];
    i_sel[N-2:0] = sel[N-2:0];
    i_sel[N-1] = 1'b0;
    DATA_LEN = N;
    SEL_LEN = N-1;
    for (TREE_DEPTH=log2N-1; TREE_DEPTH>=0;
        TREE_DEPTH=TREE_DEPTH-1)
        begin
            SEL_LEN = (DATA_LEN+1)/2;
            S = SEL_LEN-1;

```

```

    J = (DATA_LEN+1)/2;
    J = J-1;
    if (even(DATA_LEN))
    for (I=DATA_LEN-1; I>=1; I=I-2)
    begin
        result[J] = mux_2_1(i_sel[I-1], {i_data[I],
            i_data[I-1]});
        temp_sel[S] = |{i_sel[I-1], i_sel[I]};
        J = J-1;
        S = S-1;
    end
    else
    begin
    for (I=DATA_LEN-1; I>=2; I=I-2)
    begin
        result[J] = mux_2_1(i_sel[I-1], {i_data[I],
            i_data[I-1]});
        temp_sel[S] = |{i_sel[I-1], i_sel[I]};
        J = J-1;
        S = S-1;
    end
        result[0] = i_data[0];
        temp_sel[0] = i_sel[0];
    end
    i_data[N-1:0] = result[N-1:0];
    i_sel[N-1:0] = temp_sel[N-1:0];
    DATA_LEN = (DATA_LEN+1)/2;
end
mux_tree_func = result[0];
end
endfunction

always @(sel or data_in)
begin
    data_out <= mux_tree_func(sel, data_in);
end
endmodule

```

Example 3-15 VHDL for Multiplexer Tree

```

library IEEE;
use IEEE.std_logic_1164.all;
entity mux_tree is
generic (N: natural := 4);
port (sel: in std_logic_vector(N downto 0);
      data_in: in std_logic_vector(N+1 downto 0);
      data_out: out std_logic);
end mux_tree;
architecture one of mux_tree is
function XOR_tree_func...
  -- See Example 3-11 on page 3-20 for XOR_tree_func source
end;
function mux_2_1(sel: std_logic; input: std_logic_vector)
  return std_logic is
variable result: std_logic;
variable i_input: std_logic_vector(1 downto 0);
begin
  i_input := input;
  if sel = '1' then
    result := i_input(0);
  else
    result := i_input(1);
  end if;
  return result;
end;

function mux_tree_func(sel, data: std_logic_vector)
  return std_logic is
variable result : std_logic;
variable upper_tree, lower_tree : std_logic;
variable i_sel : std_logic_vector(sel'LENGTH-1 downto 0);
variable i_data : std_logic_vector(data'LENGTH-1downto 0);
variable final_sel : std_logic;
variable val : std_logic_vector(1 downto 0);
variable SEL_LEN, DATA_LEN, MID : natural;
begin
  i_sel := sel;
  i_data := data;
  DATA_LEN := i_data'LENGTH;
  SEL_LEN := i_sel'LENGTH;
  if SEL_LEN = 0 or DATA_LEN = 0 then
  elsif SEL_LEN = 1 then
    result := mux_2_1(i_sel(0), i_data);
  elsif SEL_LEN = 2 then
    upper_tree := mux_2_1(i_sel(1), i_data(2 downto 1));
    val := (upper_tree, i_data(0));
    result := mux_2_1(i_sel(0), val);

```

```

elseif SEL_LEN = 3 and DATA_LEN = 3 then
    upper_tree := mux_2_1(i_sel(2), i_data(2 downto 1));
    val := (upper_tree, i_data(0));
    final_sel := i_sel(1) OR i_sel(0);
    result := mux_2_1(final_sel, val);
elseif SEL_LEN = 3 and DATA_LEN = 4 then
    upper_tree := mux_2_1(i_sel(2), i_data(3 downto 2));
    lower_tree := mux_2_1(i_sel(0), i_data(1 downto 0));
    val := (upper_tree, lower_tree);
    final_sel := i_sel(1) OR i_sel(0);
    result := mux_2_1(final_sel, val);
else
    MID := (DATA_LEN + 1)/2 + i_data'RIGHT;
    upper_tree := mux_tree_func(i_sel(i_sel'LEFT downto MID),
        i_data(i_data'LEFT downto MID));
    lower_tree := mux_tree_func(i_sel(MID-2 downto i_sel'RIGHT),
        i_data(MID - 1 downto i_data'RIGHT));
    val := (upper_tree, lower_tree);
    final_sel := XOR_tree_func(i_sel(MID - 1 downto 0));
    result := mux_2_1(final_sel, val);
end if;
return result;
end;

begin
    data_out <= mux_tree_func(sel, data_in);
end one;

```

Figure 3-10 shows the structure implied by Example 3-14 and Example 3-15.

Figure 3-10 Structure Implied by Multiplexer Tree Example

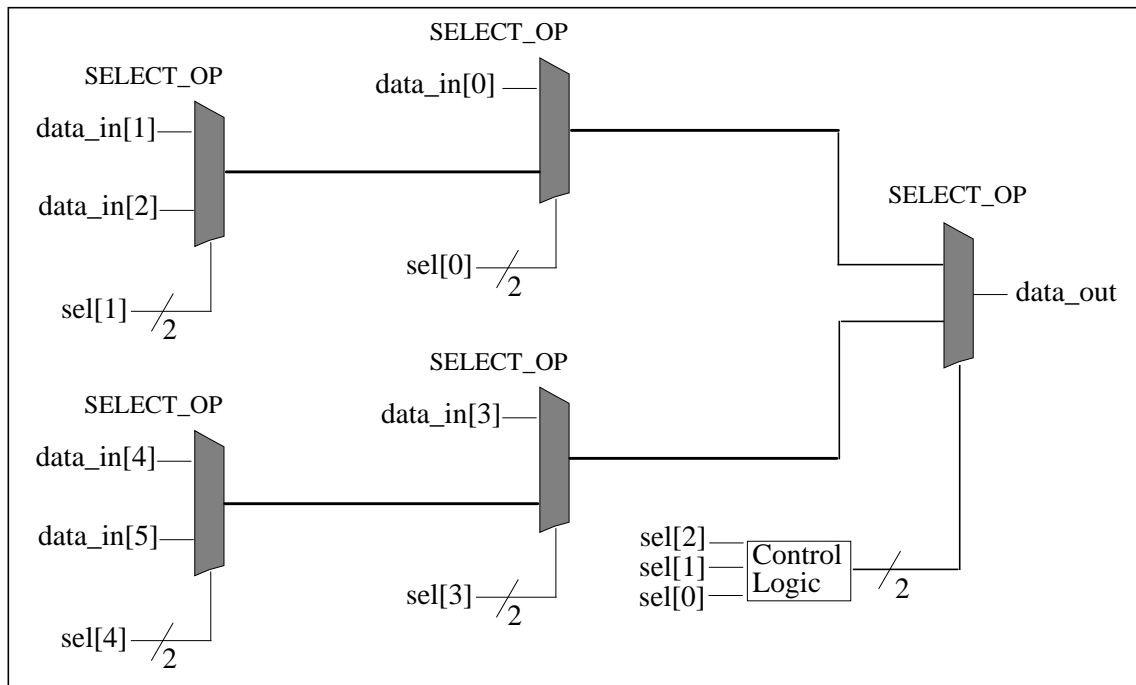


Table 3-7 and Figure 3-11 show timing results for different-size multiplexer chains and trees, using the coding styles described previously.

Table 3-7 Timing Results for Various Multiplexer Coding Styles

# of Muxes	3	4	5	6	7	8
Chain	0.72	1.18	1.3	1.76	1.88	2.34
Tree	0.72	1.01	1.01	1.09	1.29	1.38

Figure 3-11 Multiplexer Timing Versus Number of Multiplexers


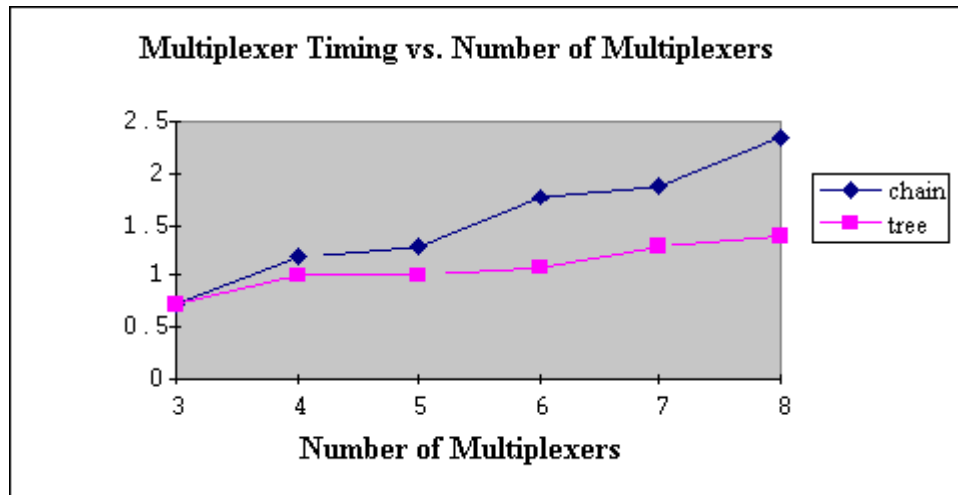


Table 3-8 and Figure 3-12 show area results for different-size multiplexer chains and trees, using the coding styles described previously.

Table 3-8 Multiplexer Area Versus Number of Multiplexers

# of Muxes	3	4	5	6	7	8
Chain	14	16	22	24	30	32
Tree	14	23	24	27	32	40

Figure 3-12 Multiplexer Area Versus Number of Multiplexers

 

From this data, it is apparent that the tree version is better with respect to timing (as expected) but a little worse with respect to area. To optimize your HDL for timing, use the tree version. If area is of greater concern, use the chain version.

A late arriving signal can also indicate the need for a chain structure. For example, if `data_in[0]` is a late arriving input, the chain structure shown in Figure 3-9 is the better startpoint.

