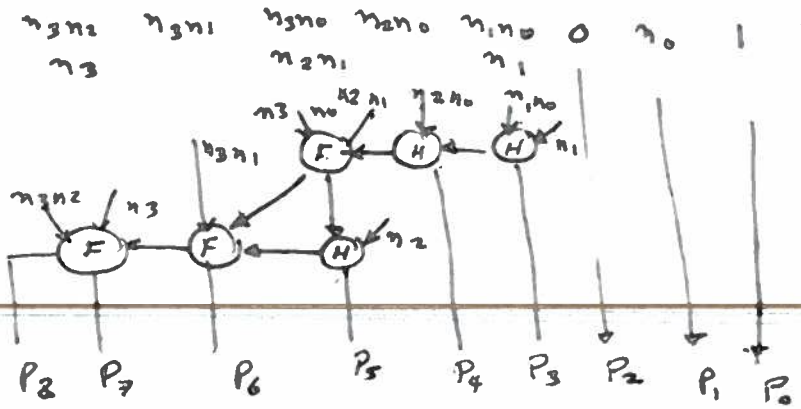


Q1


$$N = \begin{matrix} n_3 & n_2 & n_1 & n_0 \\ n_3 & n_2 & n_1 & n_0 \end{matrix}$$

$$\begin{matrix} n_3 n_0 & n_2 n_0 & n_1 n_0 & n_0 n_0 \\ n_3 n_1 & n_2 n_1 & n_1 n_1 & n_0 n_1 \\ n_3 n_2 & n_2 n_2 & n_1 n_2 & n_0 n_2 \\ n_3 n_3 & n_2 n_3 & n_1 n_3 & n_0 n_3 \end{matrix}$$

$$\begin{matrix} n_3 n_2 & n_3 n_1 & n_3 n_0 & n_2 n_0 & n_1 n_0 & 0 & n_0 & 0 & \swarrow 2N^2 \\ n_3 & & n_2 n_1 & & n_1 & & & & 1 + 1 \end{matrix}$$




$$N = 1011 = 11 \quad 2N^2 + 1 = 243$$

 

 Q 2

This implementation can be done in several ways, in terms of how to divide the 8-bit. Below we give implementation by using two 4-bit carry skip Adder




Critical Path
Carry skip = $8 * \tau_{FA} + 2 \tau_{AND} + 2 \tau_{MUX} = 8 * 3 + 2 \tau_{gate} + 3 * 2 \tau_{gate} = 32 \tau_{gate}$

Critical Path
Carry Ripple = $8 * \tau_{FA} = 8 * 3 = 24 \tau_{gate}$

Area of Carry skip = $8 * A_{FA} + 2 A_{AND} + 2 A_{MUX}$
 $= 8 * 5 A_{gate} + 2 A_{gate} + 2 * 3 A_{gate}$
 $= 48 A_{gate}$

 Area of Carry Ripple = $8 * A_{area FA}$
 $= 8 * 5 A_{gate} = 40 A_{gate}$




Full Adder
 Delay = $3 \tau_{gate}$
 Area = $5 A_{gate}$



Mux
 Delay $3 \tau_g$
 Area = $4 \tau_g$
 neglect inputs

Q3

Oct 2012

 

Present state			Next state		
y_3	y_2	y_1	y_3^+	y_2^+	y_1^+
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	0	1	1
1	1	1	0	1	1

y_3	$y_2 y_1$	00	01	11	10
0	0	0	0	1	1
1	0	0	0	1	1

$y_1^+ = y_2 = D_1$

y_3	$y_2 y_1$	00	01	11	10
0	0	0	0	0	0
1	0	1	1	1	1

$y_2^+ = y_3 = D_2$

y_3	$y_2 y_1$	00	01	11	10
0	0	0	0	0	0
1	0	0	0	0	0

$y_3^+ = 0 = D_3$

Using D Flip Flop

$y_3^+ = 0 = D_3$
 $y_2^+ = y_3 = D_2$
 $y_1^+ = y_2 = D_1$

