

Answer all Questions.

All questions carry equal marks.

Exam Duration 3 hour

No books or papers are allowed.

Examiner: Asim J. Al-Khalili

=====

### Question 1

Using **Boolean algebra**, minimize the following function:

a)  $F(A,B,C,D) = ABCD + (ABD)' + ABC'D$

b) Given  $f(x,y,z) = xy + xz' + yz$


i) Implement  $f$  in **NOR-NOR** format

ii) Implement  $f$  in **AND-OR-INVERT** format

**Obtain optimum implementation.**
 
### Question 2

Design a combinational circuit decoder that examines a BCD digit and displays a letter "L" if the digit was less than or equal 5. Use the Display unit shown below. Implement the circuit using minimum 2\*1 MUXes.



### **Question 3**

- a) Design a Half Subtractor.
- b) Design a Full Subtractor using two Half Subtractors.
- c) Using two 4 \* 1 multiplexers implement the Full Subtractor

### **Question 4**


Design a BCD adder that adds two BCD digits and produces a sum digit in BCD. You may use 4-bit binary adders for your design. Give the circuit diagram.

### **Question 5**

Design a sequential circuit with two JK flip flops A & B and two inputs E & F. If E=0, the circuit remains in the same state regardless of the value of F. When E=1 and F=1, the circuit goes through the state transition from 00 to 01 to 10 to 11, back to 00 and repeats. When E=1 and F=0, the circuit goes through the state transitions from 00 to 11, to 10 to 01, back to 00 and repeats.
 
## Question 6

Analyze the circuit below fully. Derive the Transition Table, Excitation Table, State Diagram and the Output. Explain the function of the circuit.



# SOLUTION

## COEN312, DEC4 2008

Q1.

a.

$$\begin{aligned}
 F(A,B,C,D) &= ABCD + (ABD)' + ABC'D \\
 &= ABD(C+C') + (ABD)' = ABD + (ABD)' = 1
 \end{aligned}$$

OR

$$\begin{aligned}
 &= ABCD + (ABD)' + ABC'D \\
 &= BCD + A' + B' + D' + BC'D \\
 &= CD + A' + B' + D' + C'D \\
 &= C + A' + B' + D' + C'D \\
 &= A' + B' + D' + C + D \\
 &= 1
 \end{aligned}$$


b.

$$\begin{aligned}
 f(x,y,z) &= xy + xz' + yz \\
 &= xy(z+z') + xz' + yz \\
 &= xyz + xyz' + xz' + yz \\
 &= xz' + yz
 \end{aligned}$$

i)

f=	Z \ XY	00	01	11	10
	0	0	0	1	1
	1	0	1	1	0


$$f = (x+z).(y+z')$$

 

ii)

f=	Z \ XY	00	01	11	10
	0	1	1	0	0
	1	1	0	0	1

$$f = (x'z') + (y'z)$$

 

Q2.

Segments 'beg' has to be on in order to have 'L' on the seven-segments display.


	A	B	C	D		a	b	c	d	e	f	g
0	0	0	0	0		0	1	0	0	1	0	1
1	0	0	0	1		0	1	0	0	1	0	1
2	0	0	1	0		0	1	0	0	1	0	1
3	0	0	1	1		0	1	0	0	1	0	1
4	0	1	0	0		0	1	0	0	1	0	1
5	0	1	0	1		0	1	0	0	1	0	1
6	0	1	1	0		0	0	0	0	0	0	0
7	0	1	1	1		0	0	0	0	0	0	0
8	1	0	0	0		0	0	0	0	0	0	0
9	1	0	0	1		0	0	0	0	0	0	0

$a=c=d=f=0$

$b=e=g = A'B'+A'C'$   
 $=A'(B'+C')$

f=

AB\CD	00	01	11	10
00	1	1	1	1
01	1	1	0	0
11	X	X	X	X
10	0	0	0	X

 

Q3.

	For the half-subtractor,				For the full-subtractor,						
a.	a	b		D	B	b.	a	b	B <sub>-</sub>	D	B
	0	0		0	0		0	0	0	0	0
	0	1		1	1		0	0	1	1	1
	1	0		1	0		0	1	0	1	1
	1	1		0	0		0	1	1	0	1
							1	0	0	1	0
							1	0	1	0	0
							1	1	0	0	0
							1	1	1	1	1
	$D = (a \oplus b)$										
	$B = \overline{ab}$										

The K-map tables give:

$$D = \begin{array}{c|cccc} b \backslash ab & 00 & 01 & 11 & 10 \\ \hline 0 & 0 & 1 & 0 & 1 \\ \hline 1 & 1 & 0 & 1 & 0 \end{array}$$



$$D = (a \oplus b \oplus b\_)$$

$$= \bar{a}\bar{b}\bar{b}\_ + \bar{a}b\bar{b}\_ + a\bar{b}\bar{b}\_ + ab\bar{b}\_$$

$$B = \begin{array}{c|cccc} b \backslash ab & 00 & 01 & 11 & 10 \\ \hline 0 & 0 & 1 & 0 & 0 \\ \hline 1 & 1 & 1 & 1 & 0 \end{array}$$

$$D = \bar{a}b + b\_ (a \oplus b)$$


$$= \bar{a}b + b\_ab + b\_ \bar{a}b$$

  

Q4.


The algorithm to do binary addition of two BCD numbers, with the result in BCD, involves a binary adder to do the actual arithmetic operation along with another adder to offset the result whenever the binary sum exceeds the BCD range, which is from 0 to 9. When this happens, the addition is scaled up by 6. The operation has to take care of the carry-out which will be asserted whenever the BCD range is exceeded or the actual binary addition generates a carry. The Boolean expression for the carry bit is:

$$C = K + Z_8Z_4 + Z_8Z_2$$

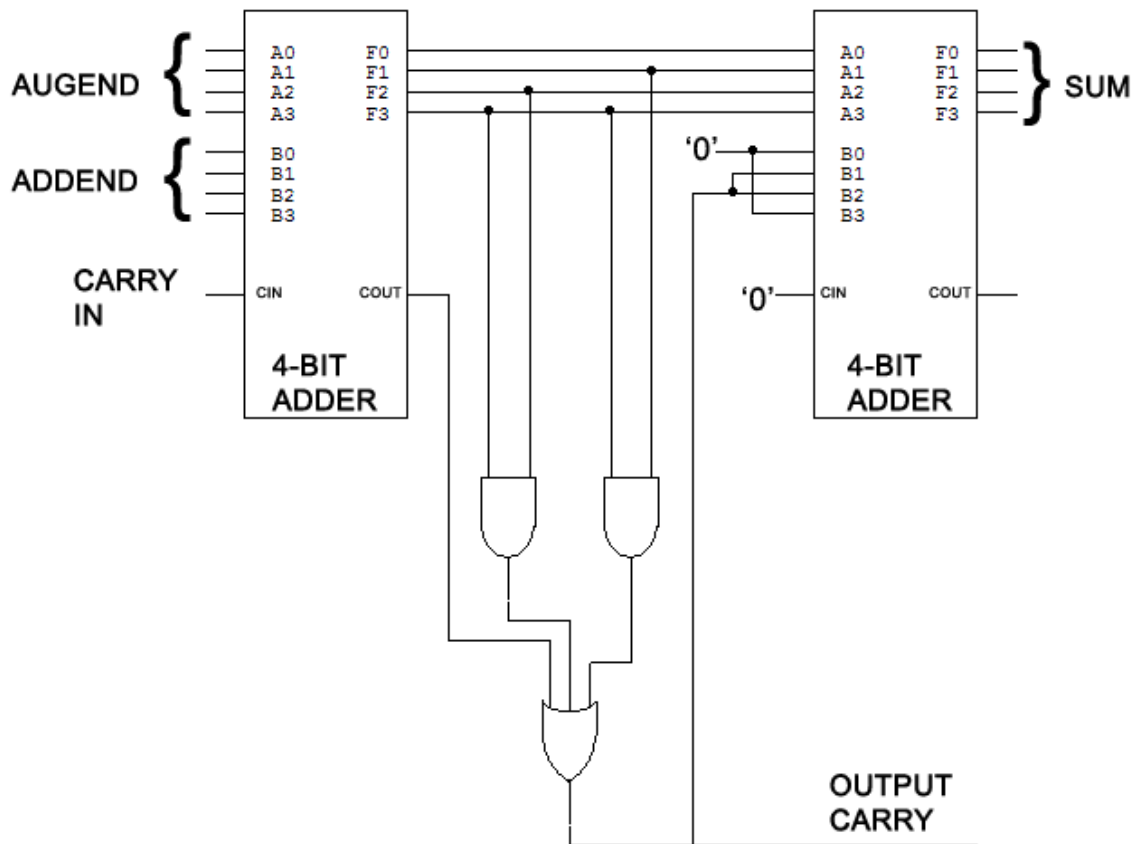

Q5.

State Diagram:

 

State Transition Table:


Present Y1 Y0	Next			
	EF 00	01	10	11
00	00	00	11	01
01	01	01	00	10
10	10	10	01	11
11	11	11	10	00

K-Maps for next state equations:

$$Y_1^+ = y_1 y_0 \backslash EF$$

	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	1	1	0	1
10	1	1	1	0

 
$$Y_1^+ = \bar{E}y_1 + Fy_1\bar{y}_0 + \bar{F}y_1y_0 + EF\bar{y}_1y_0 + E\bar{F}\bar{y}_1\bar{y}_0$$



$$Y_0^+ = y_1 y_0 \backslash EF$$

	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1

$$Y_0^+ = \bar{E}y_0 + E\bar{y}_0$$

 



Q6.

Analysis:


$$T_A = Q_A + Q_B$$

$$T_B = \overline{Q_A} + Q_B$$

State transition table:

		CLK		NEXT STATE	
$Q_A$	$Q_B$	$T_A$	$T_B$	$Q_A^+$	$Q_B^+$
0	0	0	1	0	1
0	1	1	1	1	0
1	0	1	0	0	0
1	1	1	1	0	0

State diagram:

 

Outputs are of the state itself.

This circuit is a counter “00”->“01”->“10” and back to “00”..., if ever started in “11” state, then the next state on the pulse will set state to “00”, “01” and so on.